


CSE 250 QUIZ-01

Name: Md. Bokhtiar Rahman Juboraz

ID : 20301133

Section : 03

Solution of number 1:

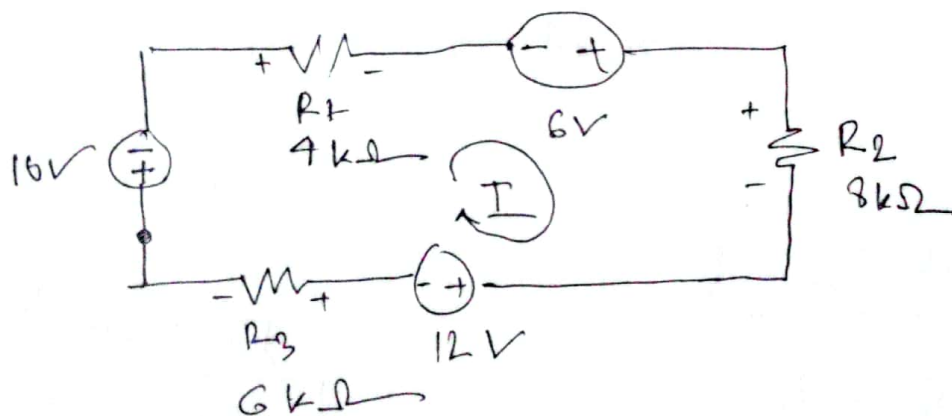

$$\begin{aligned}\text{KVL: } 10 &+ IR_1 - 6 + IR_2 + 12 + IR_3 = 0 \\ \Rightarrow 10 + 4I - 6 + 8I + 12 + 6I &= 0 \\ = 16 + 18I &= 0 \\ \Rightarrow 18I &= -16 \\ \therefore I &= -\frac{16}{18} \text{ mA}\end{aligned}$$



∴ Power in R_1 :

$$P = i^2 R_T$$

$$\begin{aligned} R_T &= R_1 + R_2 + R_3 \\ &= 4 + 8 + 6 \\ &= 18 \text{ k}\Omega. \end{aligned}$$

$$\begin{aligned} \therefore \text{Power, } P &= \left(\frac{16}{18} \right)^2 \times 18 \\ &= \frac{16^2}{18} \\ &= 14.22 \text{ mW}. \end{aligned}$$

Solution no. 02

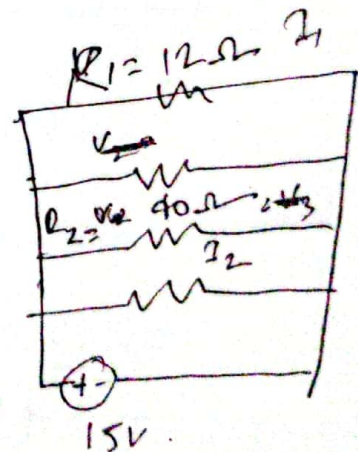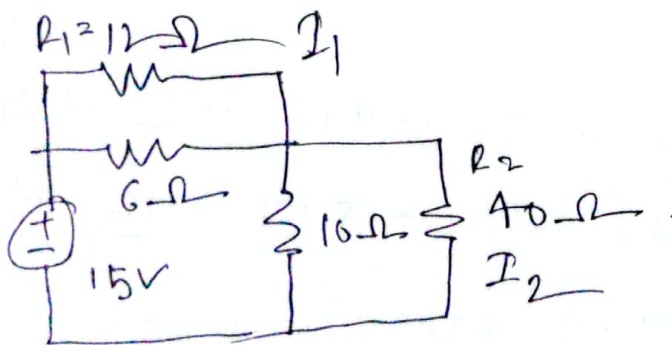

$$V_1 = \frac{R_1}{R_T} \times 10V$$

$$= \frac{12}{0.375} \times 10 = 2.66 \times 10 = 26.67V.$$

(Ans)

Current through 40Ω :

$$I_2 = \frac{R_1}{R_2} \times I_1.$$

$$= \frac{2.67}{40} \times \cancel{I_1} \times \frac{V}{R_1}$$

$$= \frac{\cancel{R_1} 2.67}{40} \times \frac{15}{\cancel{R_1}}$$

$$= \frac{15}{40}$$

$$= \underline{\hspace{1cm}} 0.375 \text{ mA. (Ans).}$$