


CSE 250, Quiz : 02

Name: Md. Bokhtiar Rahman Jubonaz

ID : 20301197

Section: 03

Answer to the question no: 01

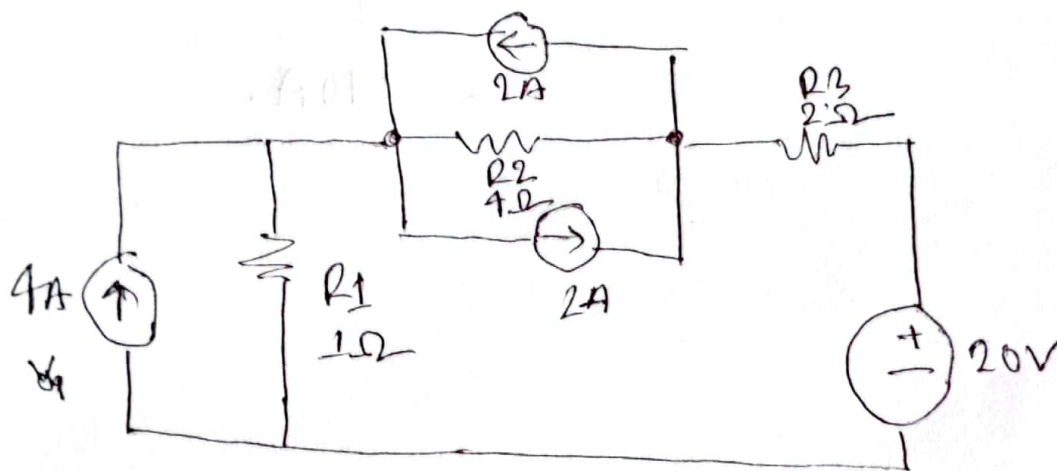


For  $R_1$ :

$$V_1 = 4 \text{ A} \cdot R_1 = 4 \text{ V.}$$

For  $R_2$ :

$$V_2 = I R_2 = (2+2) \cdot 4 = 16 \text{ V.}$$

Transformed circuit:

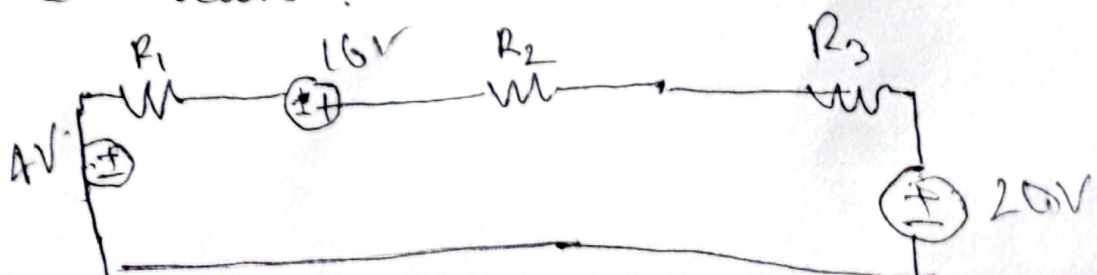


$$\text{So, } V = 4 + 16 + 20 \\ = 40V.$$

$$R_T = 1 + 4 + 2 \\ = 6 + 1 = 7 \Omega$$

$$\therefore \text{Current through } R_3: \frac{R_T}{R_3} \times 40V. \\ = \frac{7}{2} \times 40 \\ = 140A.$$



# Solution no. 02

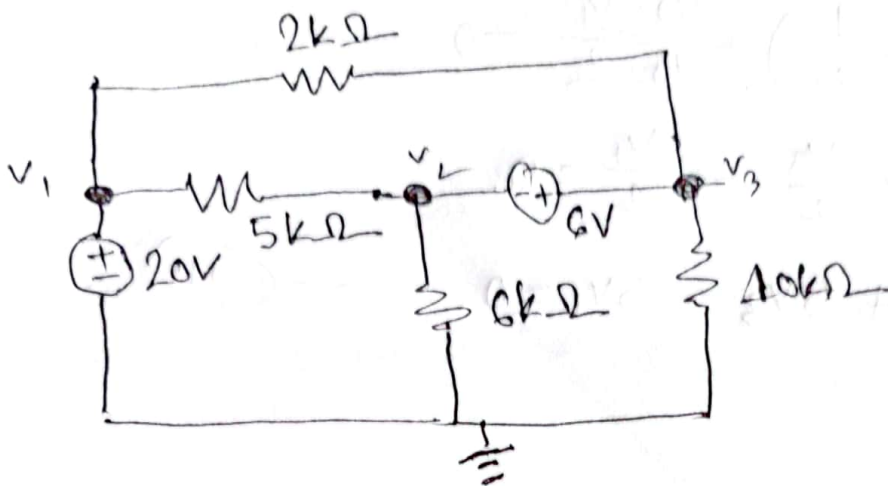

For  $V_1$  applying KVL:

$$V_1 \left( \frac{1}{2} + \frac{1}{5} \right) - \frac{V_3}{2} - \frac{V_2}{5} = 0.$$

$$\Rightarrow \frac{V_1}{2} + \frac{V_1}{5} - \frac{V_3}{2} - \frac{V_2}{5} = 0.$$

$$\Rightarrow \frac{5V_1 + 2V_1}{10} - \frac{V_3}{2} - \frac{V_2}{5} = 0, \quad \dots \text{--- (I)}$$

For  $V_2$  applying KVL:

$$V_2 \left( \frac{1}{5} + \frac{1}{6} \right) - \frac{V_1}{5} - \frac{6}{6} = 0$$

$$\Rightarrow V_2 \left( \frac{1}{5} + \frac{1}{6} \right) - \frac{V_1}{5} - 1 = 0.$$

$$\Rightarrow \frac{V_2}{5} + \frac{V_2}{6} - \frac{V_1}{5} = 1. \quad \dots \text{--- (II)}$$

$$\Rightarrow V_2 + V_2 - V_1 = 5.$$

For  $V_3$ , applying ~~KVL~~ KVL:

$$V_3 \left( \frac{1}{10} + \frac{1}{2} \right) - \frac{0}{10} - \frac{V_1}{2} = 0.$$

$$\Rightarrow \frac{V_3}{10} + \frac{V_3}{2} - \frac{V_1}{2} = 0.$$

$$\Rightarrow V_3 + 5V_3 - 5V_1 = 0.$$

— (iii) —