

BRAC UNIVERSITY
DEPT. OF COMPUTER SCIENCE AND ENGINEERING
COURSE NO.: CSE250
Circuits and Electronics Laboratory
Name: Md. Bokhtiar Rahman Juboraz
Id: 20301138


Experiment No. 1

Name Of The Experiment:


CONSTRUCTION & OPERATION OF SIMPLE ELECTRICAL CIRCUITS

PROCEDURE:


Step 1:

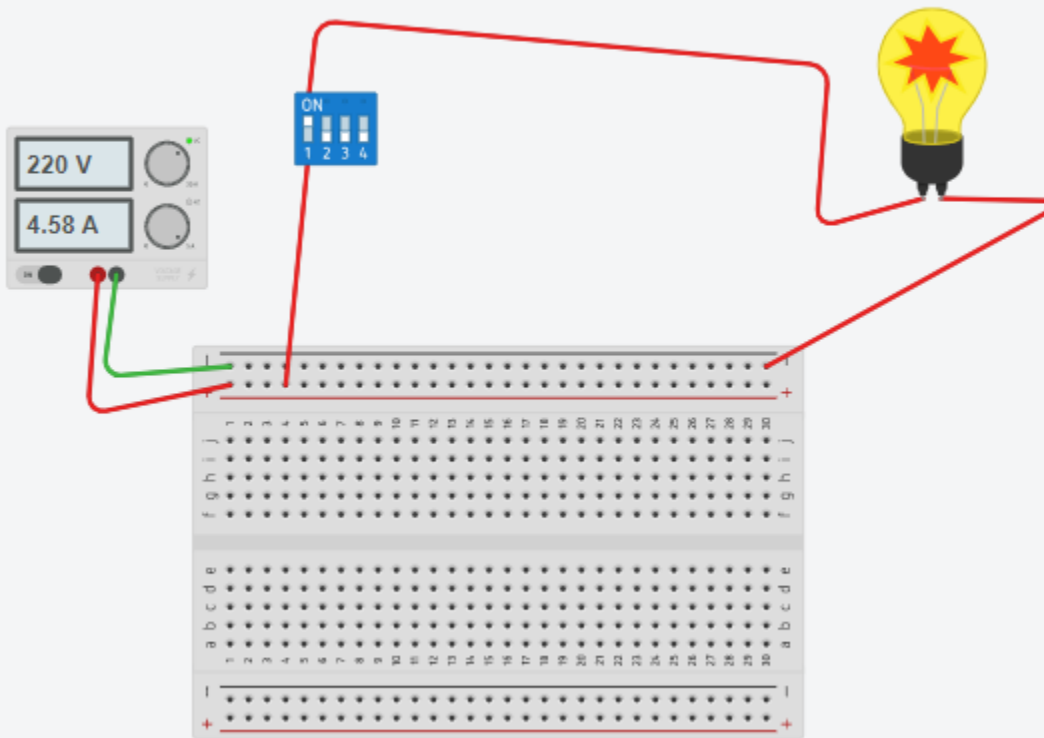


Step 2: (a)

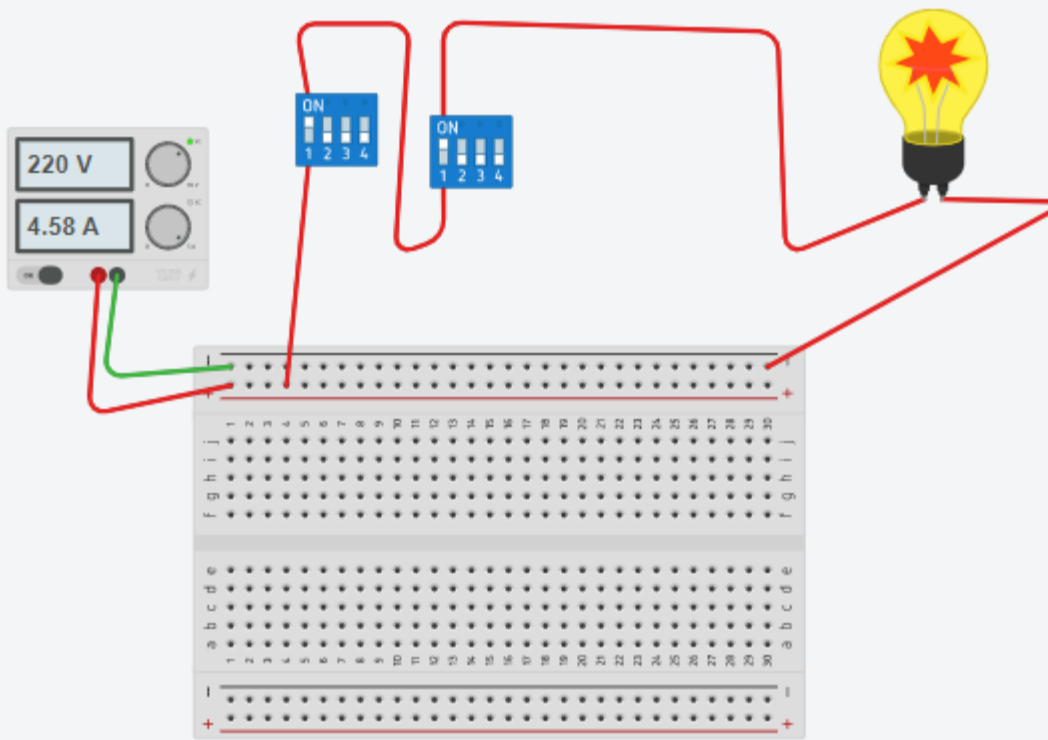


Step 2: (b)

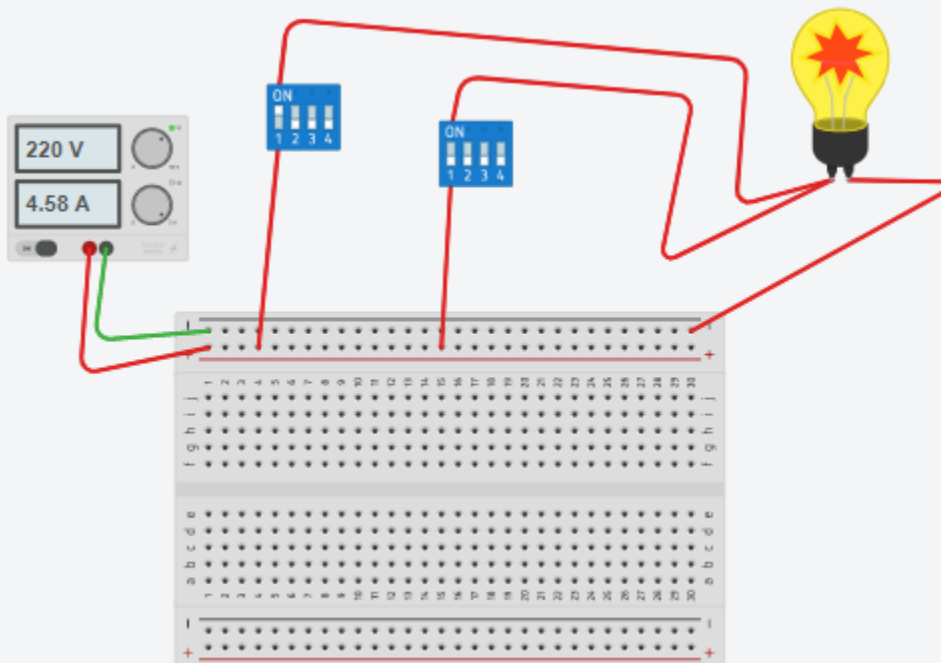


Step3 :

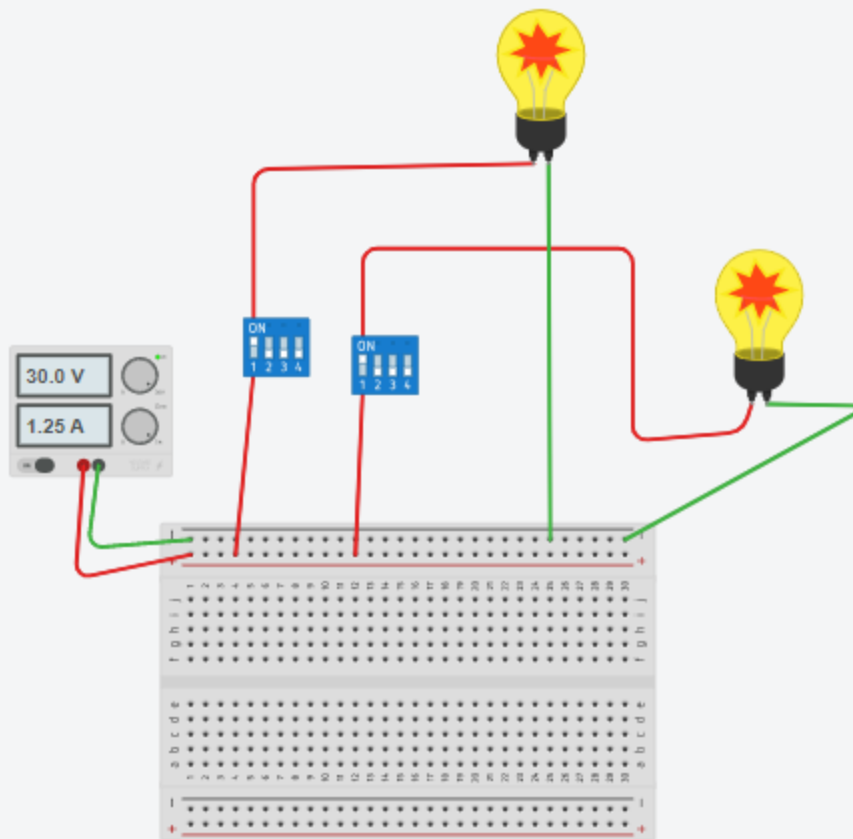

Step 4: (a)

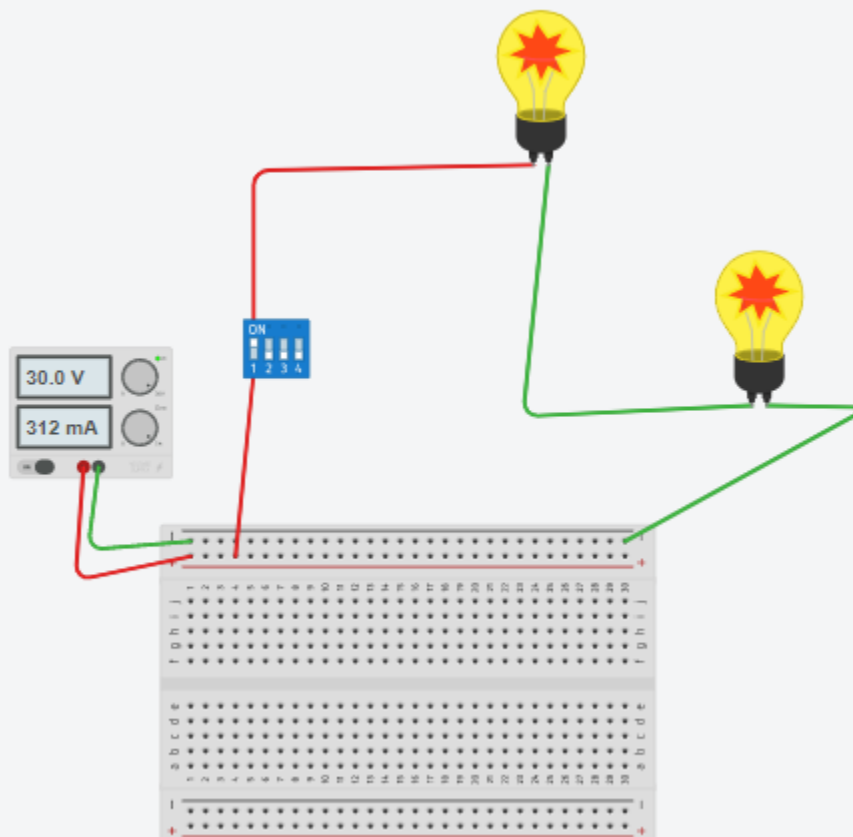

Step4: (b)

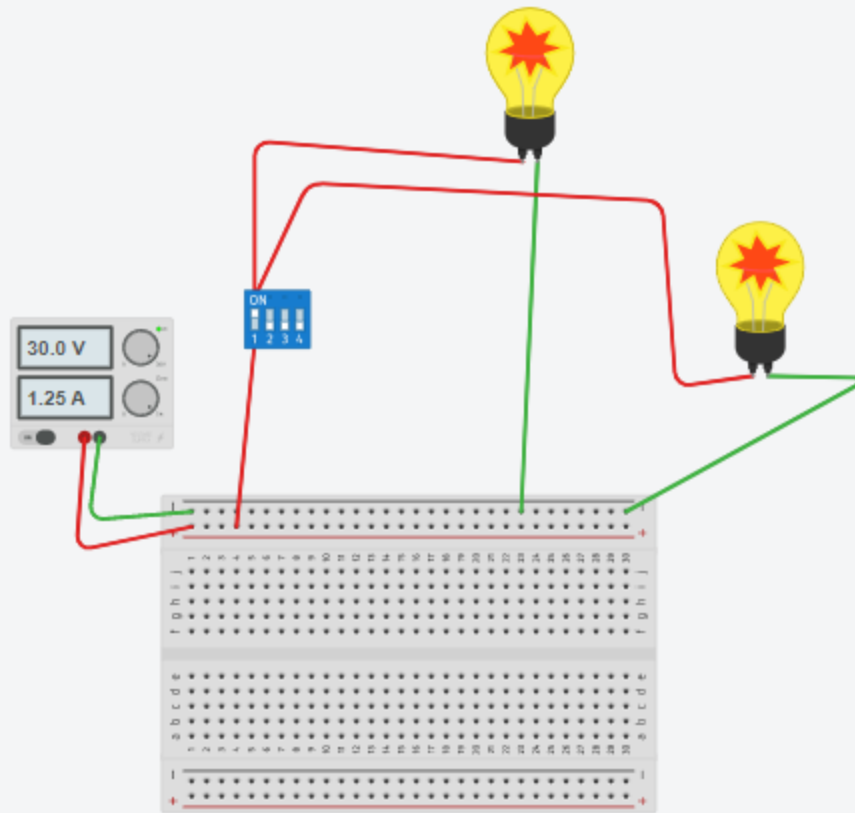

Step 5:

