



BRAC UNIVERSITY
DEPT. OF COMPUTER SCIENCE AND ENGINEERING
COURSE NO.: CSE250

Circuits and Electronics Laboratory
Name: Md. Bokhtiar Rahman Juboraz
ID: 20301138
Section: 03

Experiment No. 7


Name of the Experiment: STUDY OF TRANSIENT BEHAVIOR OF RC CIRCUIT

EXPERIMENTAL SETUP:

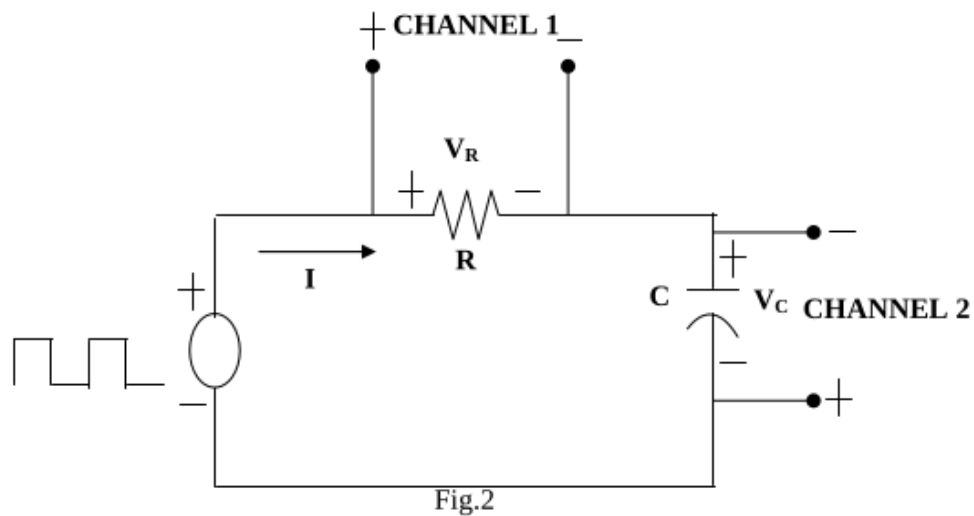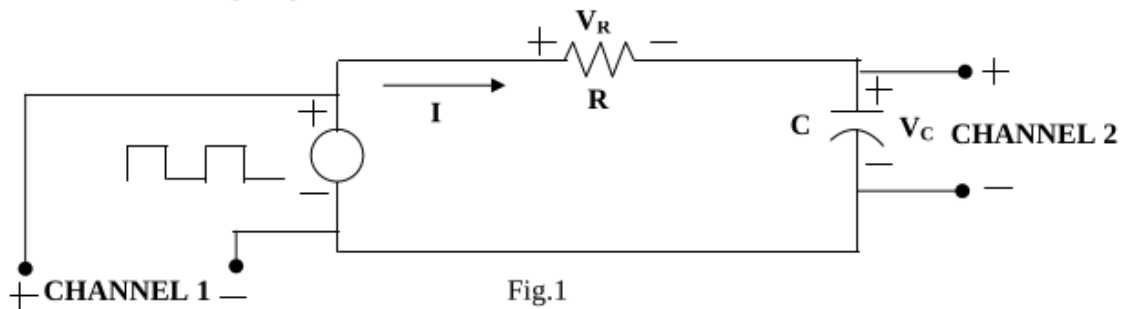

Simulations for the experiment:

For figure 1:

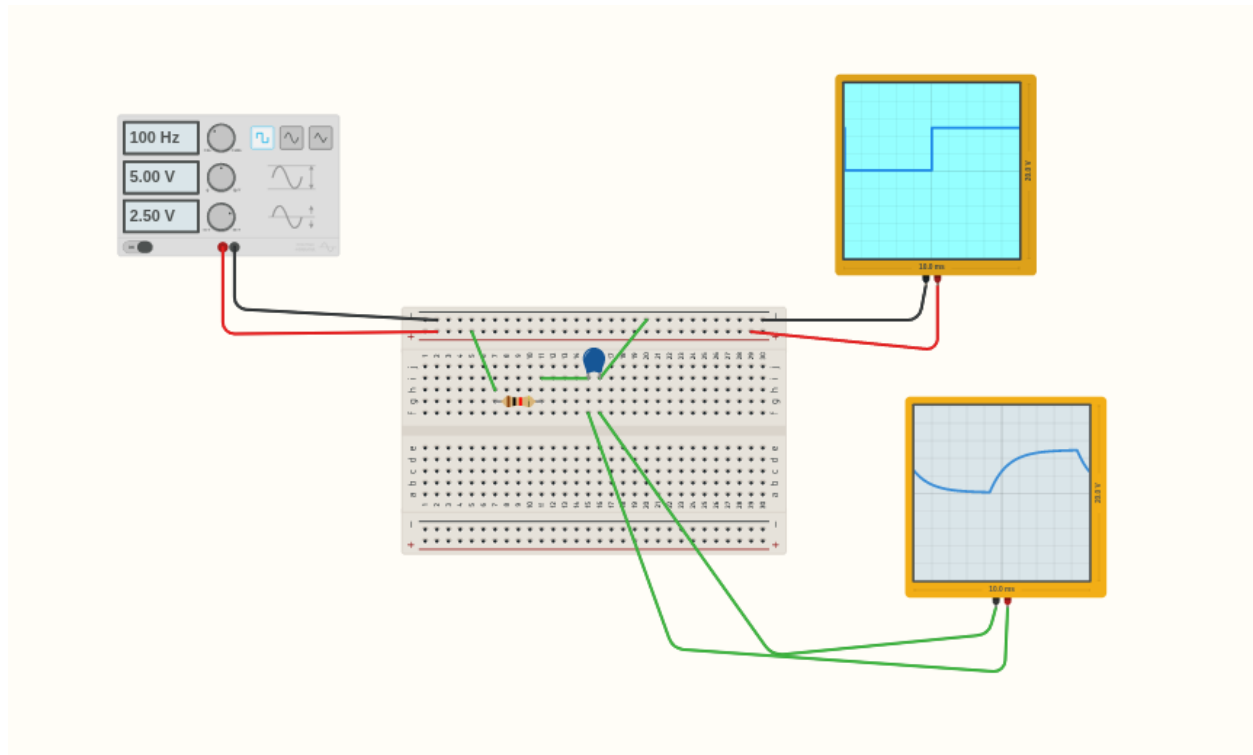

For figure 2 (inverse):

